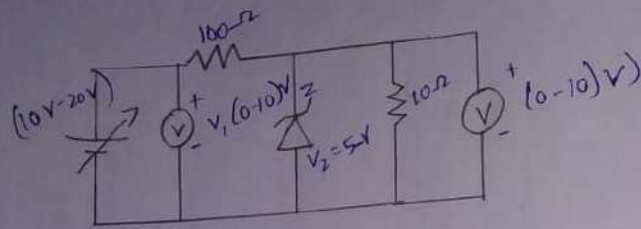



### CIRCUIT DIAGRAM:



### TABULATION:

S.No	INPUT VOLTAGE $V_1$ (V)	OUTPUT VOLTAGE $V_0$ (V)
1	+12.0	+5.14
2	+13.0	+5.16
3	+14.0	+5.17
4	+15.0	+5.17
5	+16.0	+5.18
6	+17.0	+5.19

### MODEL GRAPH:

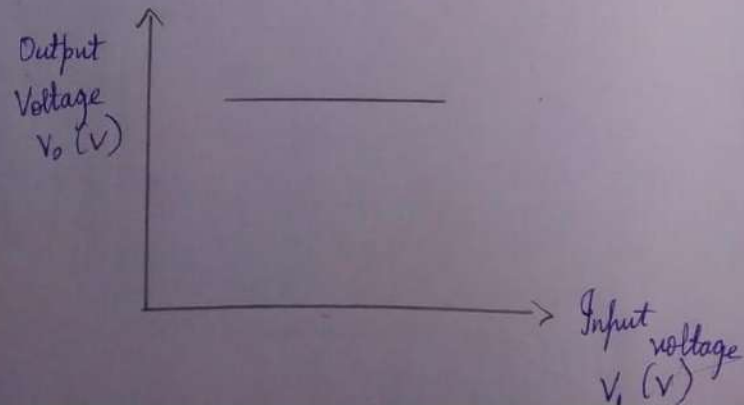

EXPT NO: 5

### ZENER DIODE AS VOLTAGE REGULATION

AIM: To simulate the line and load regulation operation Zener diode.

APPARATUS REQUIRED:  
Laptop with proteus software.

### THEORY:


A heavily doped PN Junction diode is called Zener diode. Due to heavily doped nature Zener diode works under forward bias and reverse bias conditions.

Zener diode under reverse bias condition is used as a voltage regulator. Even if the input voltage changes the output is constant. This is called line regulation.


If the load resistance changes the output voltage is constant this is called load regulation.

CIRCUITDIAGRAM:


LOAD REGULATION

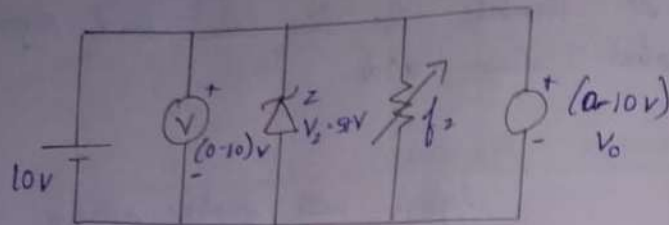
TABULATION:

S.No	LOAD RESISTANCE $R_2 (\Omega)$	OUTPUT VOLTAGE $V_o (V)$
1	100 $\Omega$	+5.19
2	200 $\Omega$	+5.20
3	300 $\Omega$	+5.20
4	400 $\Omega$	+5.20
5	500 $\Omega$	+5.20
6	600 $\Omega$	+5.21

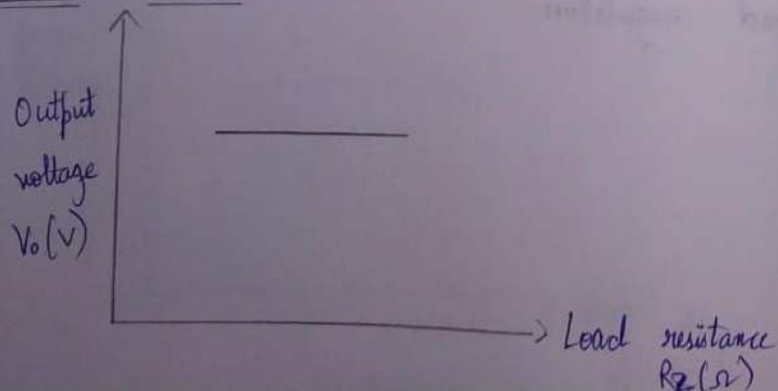
MODELDIAGRAM:PROCEDURE:

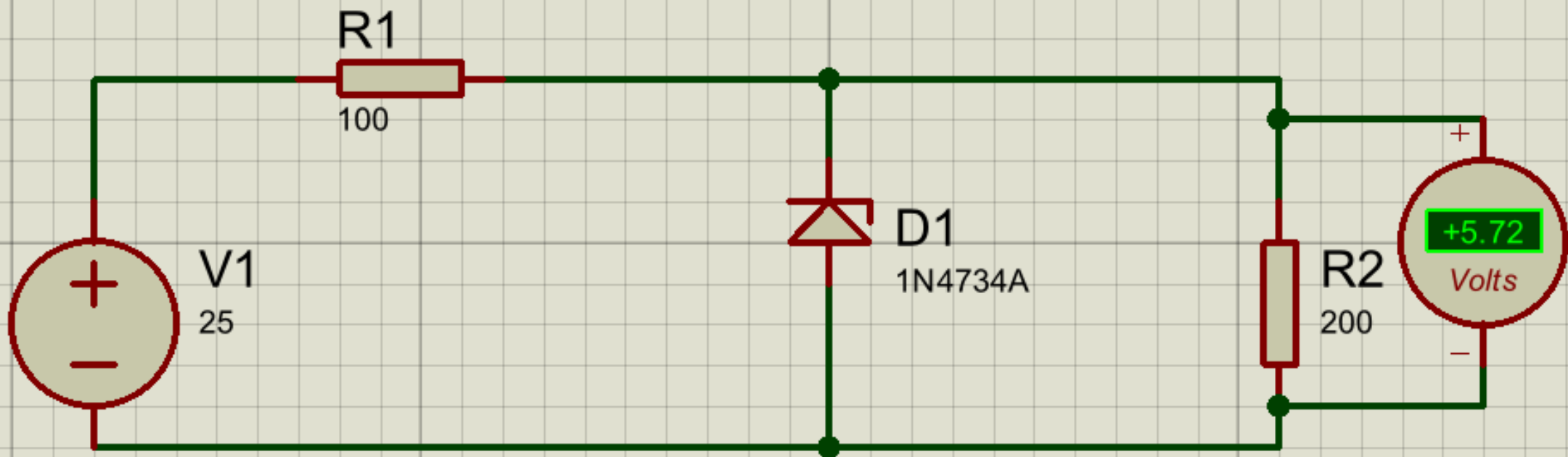1. Drag the required components from the source library.
2. Connect the components (required) as per circuit diagram.
3. For line regulation, vary the input voltage and note the output voltages in tabulation. Draw the graph between input voltage and output voltage.
4. For load regulation, vary the load resistance and note the output voltage in tabulations. Draw the graph between load resistance and output voltage.



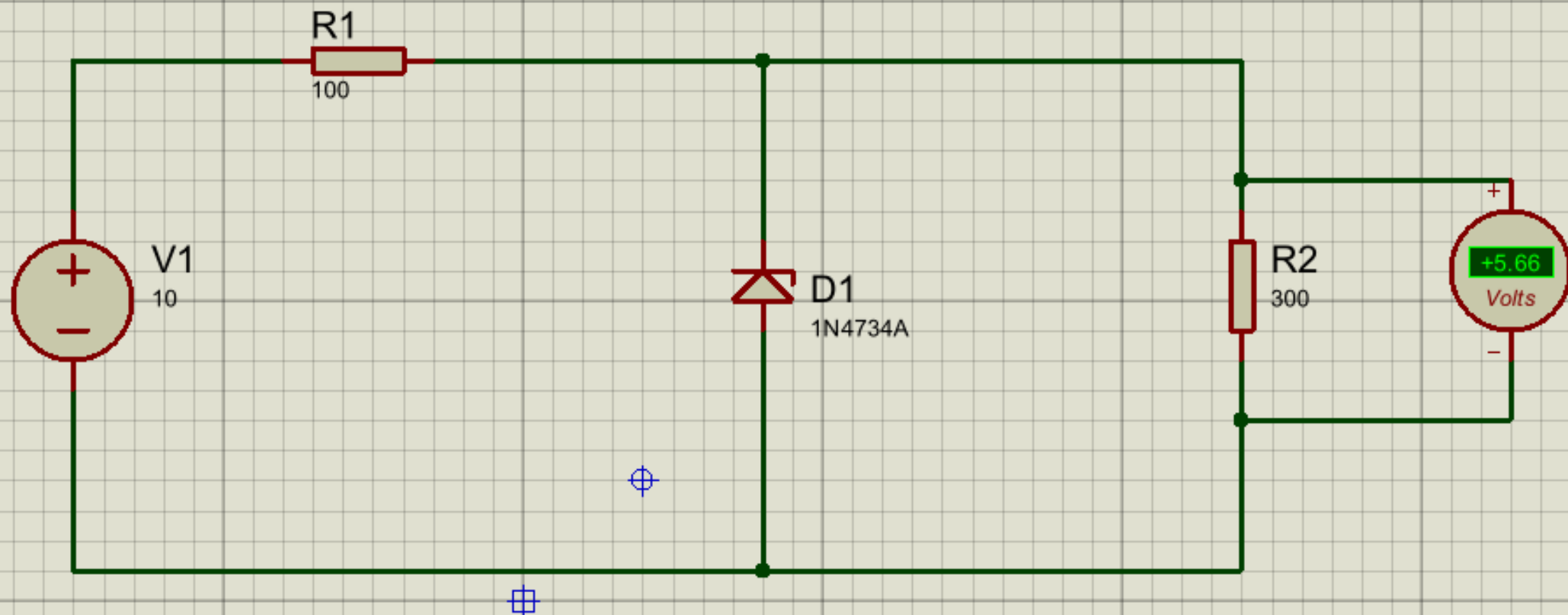

### OUTPUT:

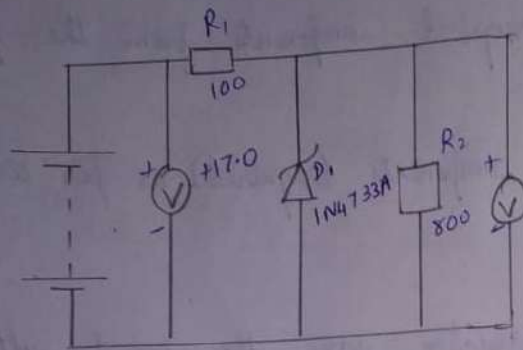

### RESULT:

Thus simulation of line load regulation operation of Zener diode is successfully completed.




# Line regulation

Scale

X-axis 1cm = 2 unit

Y-axis 1cm = 1 unit

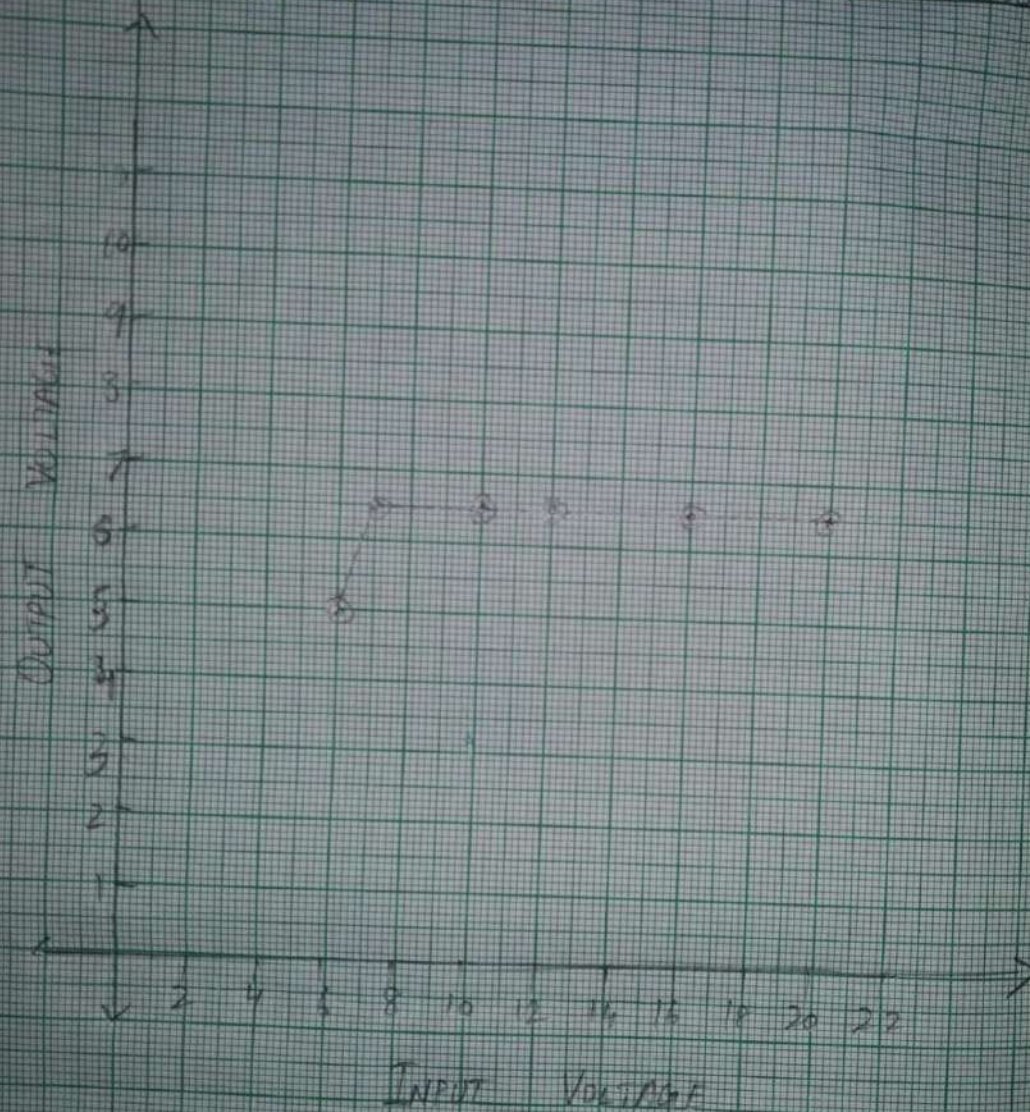



Load regulation

Scale

X-axis 1cm = 50 units

Y-axis 1cm = 1 unit

